

# Probability Hardware Assignment

Name -: Arjit Jain  
Roll no -: AI22BTECH11002

**Abstract**—Shift registers were used to create a random number generator for this assignment.

## COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K $\Omega$	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE 0  
COMPONENTS USED

1.1.1. Generate the CLOCK signal using the 555 timer circuit the figure ??

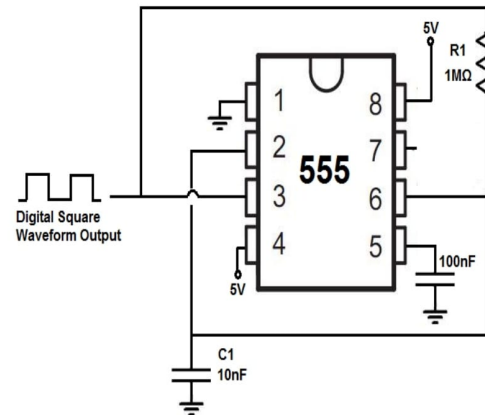


Fig. 7. Connection in 555 timer circuit

## PROCEDURE

- 1) We connected the 555 timer circuit like the figure 7
- 2) Then, we coupled the 555 timer's clock output to the D-flip flops' clock signal.
- 3) Now we make the circuit for shift registers using a 4 D-Flip flops (using two 7474 IC's)
- 4) Then we connected XOR gate (7486 IC) according to the figure 7
- 5) Then we connected the decoder (7447 IC) and connected its A,B,C,D with  $Q_0, Q_1, Q_2, Q_3$  respectively as per the figure 7
- 6) Then, in accordance with the table, we connected the seven segmented display and the decoder (7447 IC) 7 and the figure 7
- 7) Before connecting the power supply, we linked all of the independent components.

## OUTPUT

Random numbers are generated on the display.

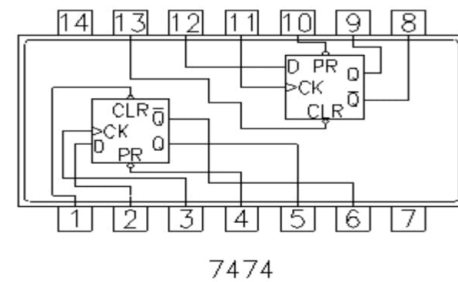


Fig. 7. Connection in 7474 IC

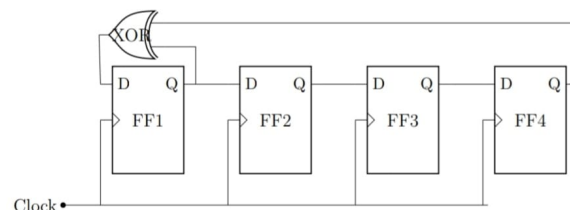


Fig. 7. Connection in XOR gate

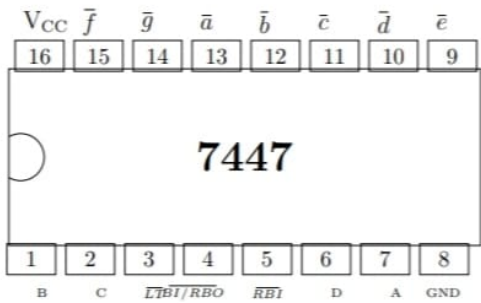


Fig. 7. Connection in Decoder gate

7447	$\bar{a}$	$\bar{b}$	$\bar{c}$	$\bar{d}$	$\bar{e}$	$\bar{f}$	$\bar{g}$
Display	a	b	c	d	e	f	g

Table 1.1.6.1

Fig. 7. Connection of seven segmented display with decoder

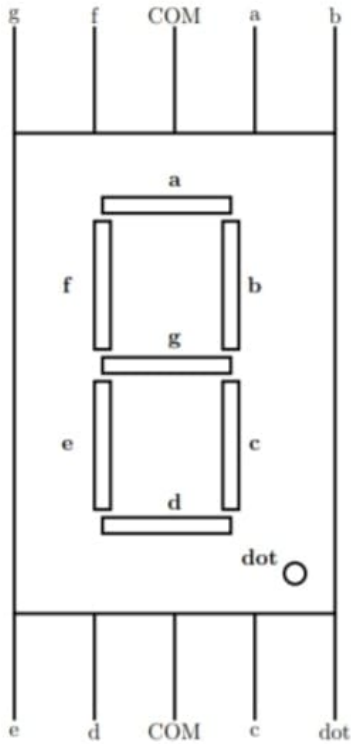


Fig. 7. Seven segmented display

Block Diagram

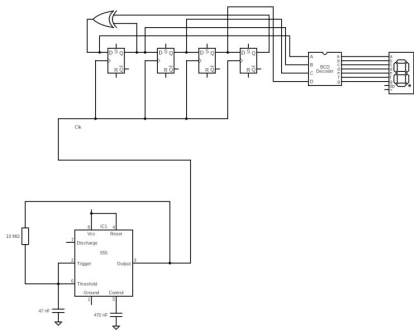


Figure 4: Block Diagram

Fig. 7. Block Diagram

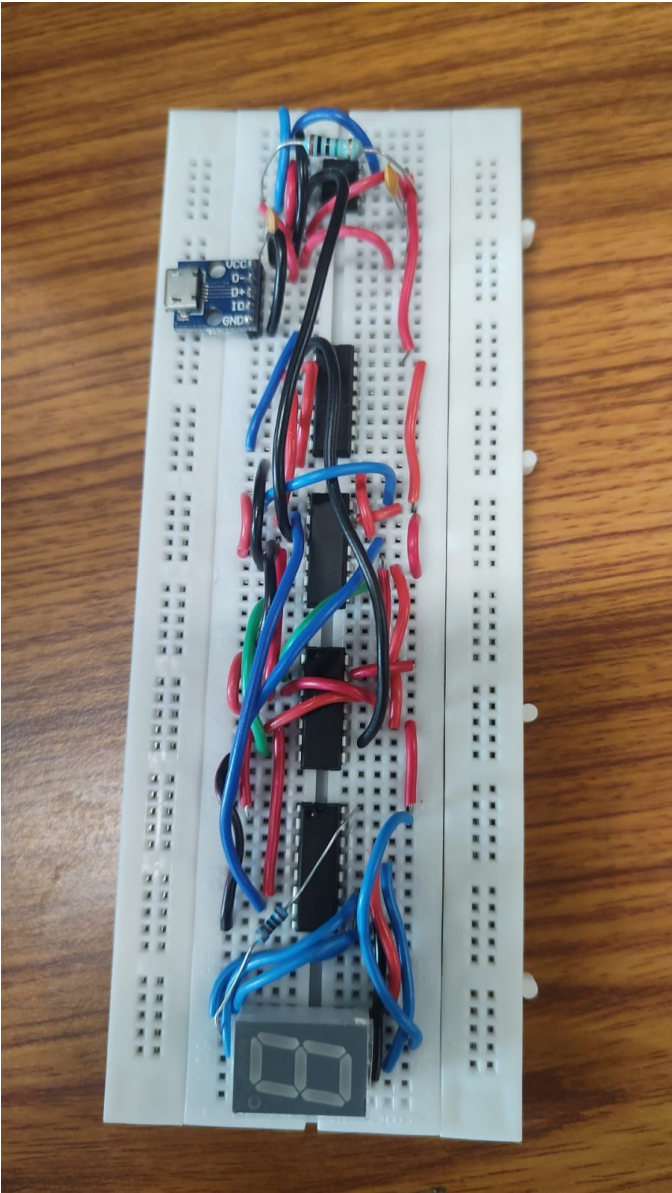


Fig. 7. output

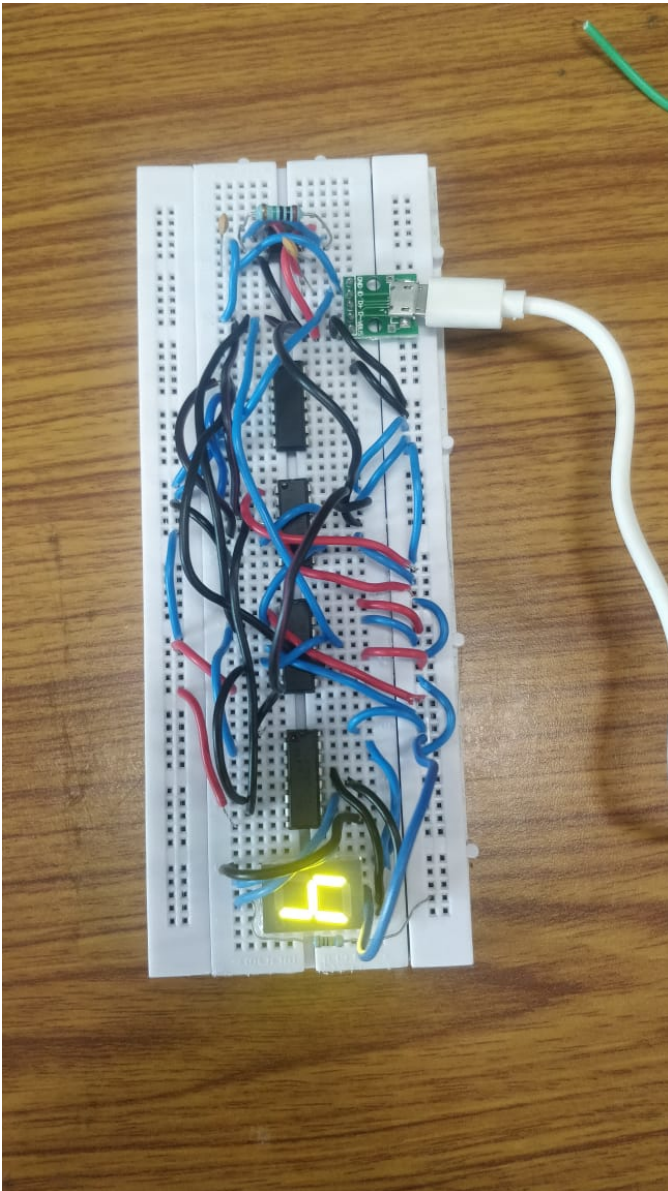


Fig. 7. output

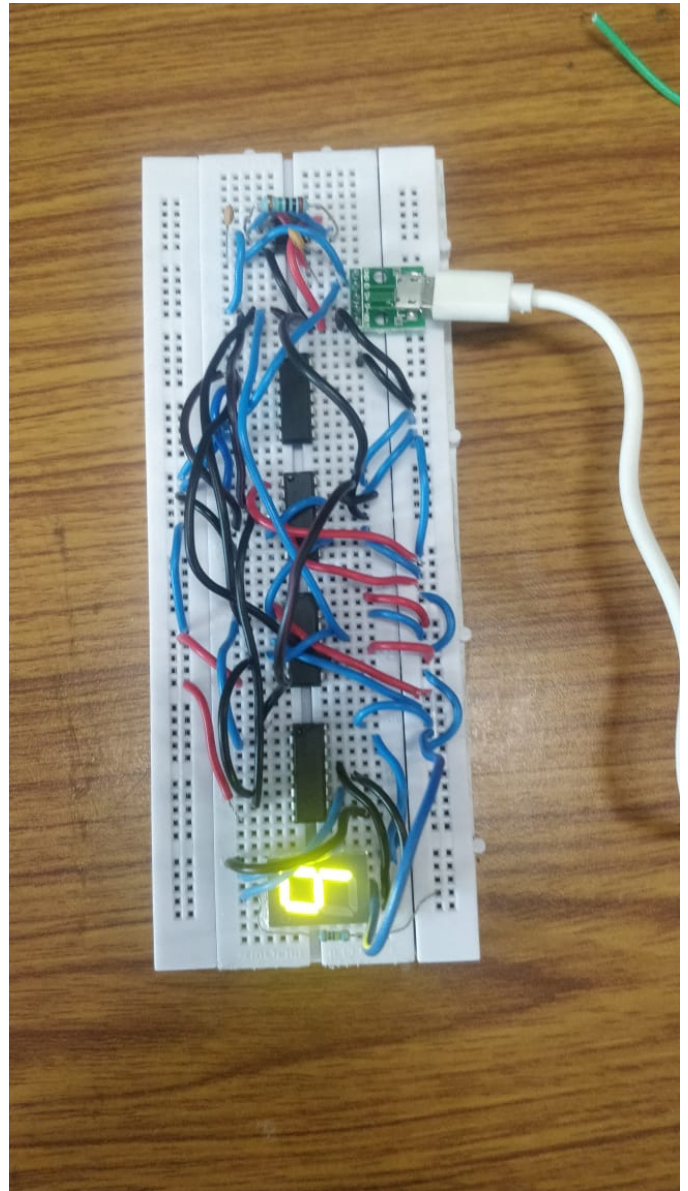


Fig. 7. output